



Birla Institute of Technology & Science, Pilani

Microprocessor Programming & Interfacing - Answer Book Part B

Only Answer in space provided

Name: _____ ID No: _____

Question No	Marks	Question No.	Marks
Q1a		Q1d	
Q1b		Q1e	
Q1c		Q1f	
Total			

Recheck Request:

5-6-2016

Q1 a

Memory Address Mapping

ROM1 - 00000H 0FFFFH
 ROM2 - 10000H 1FFFFH
 ROM3 - 20000H 2FFFFH.
 ROM4 - 30000H 3FFFFH.
 ROM5 - 40000H 4FFFFH
 RAM1 - 50000H 5FFFFH
 + all addresses.





RAM2 60000 - 6FFFFH
 RAM3 70000 - 7FFFFH.
 RAM4 80000 - 8FFFFH
 RAM5 90000 - 9FFFFH
 RAM6 A0000 - AFFFFH.
 ROM6 B0000 - BFFFFH
 ROM7 C0000 - CFFFFH.
 ROM8 D0000 - DFFFFH.
 ROM9 E0000 - EFFFFH
 ROM10 F0000 - FFFFFH

[6]

Memory Decoding



Memory Interfacing

    

Address + Data - 2M

Control Signal - 1M


Q1b

I/O Address Mapping

8255	20 - 26H
8254	40 - 46H
16550	30 - 3EH
8259	50 - 52H


[3M].

I/O Decoding

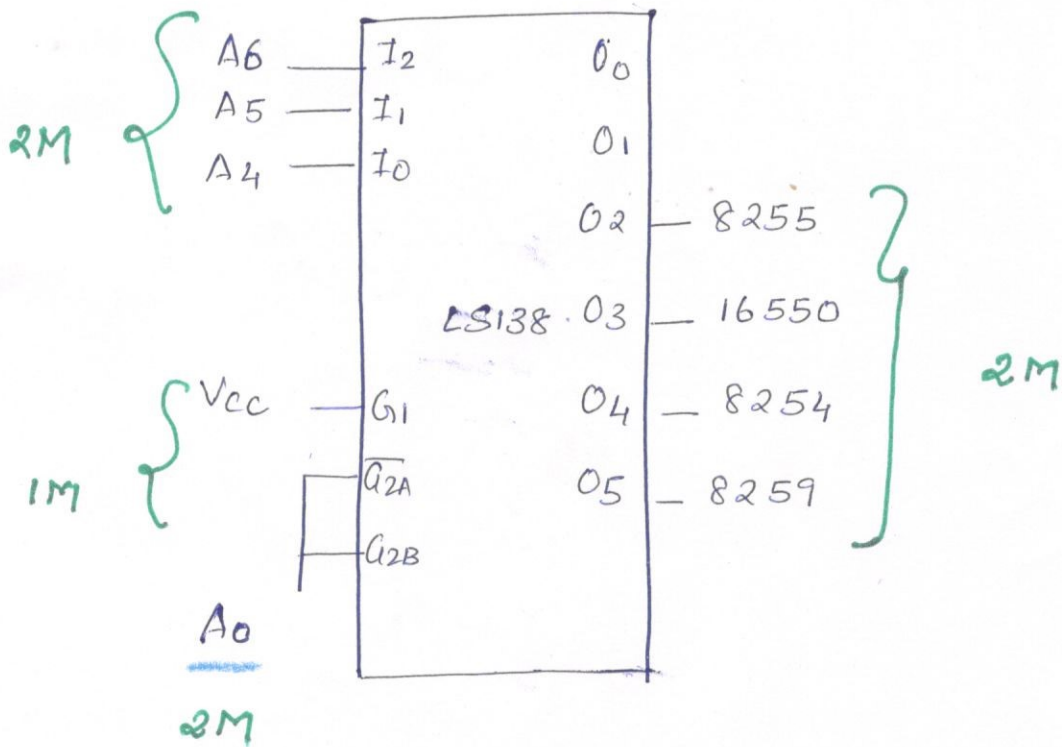

Q1C

8255 Interfacing

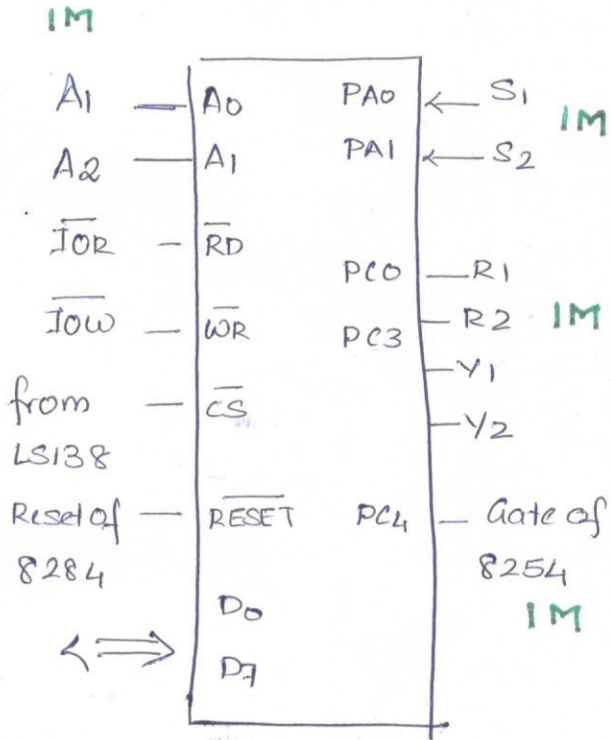


8255 Initialization

```
mov al, 10010010B.  
out 26h, al
```

IM

Q1d

8254 Interfacing

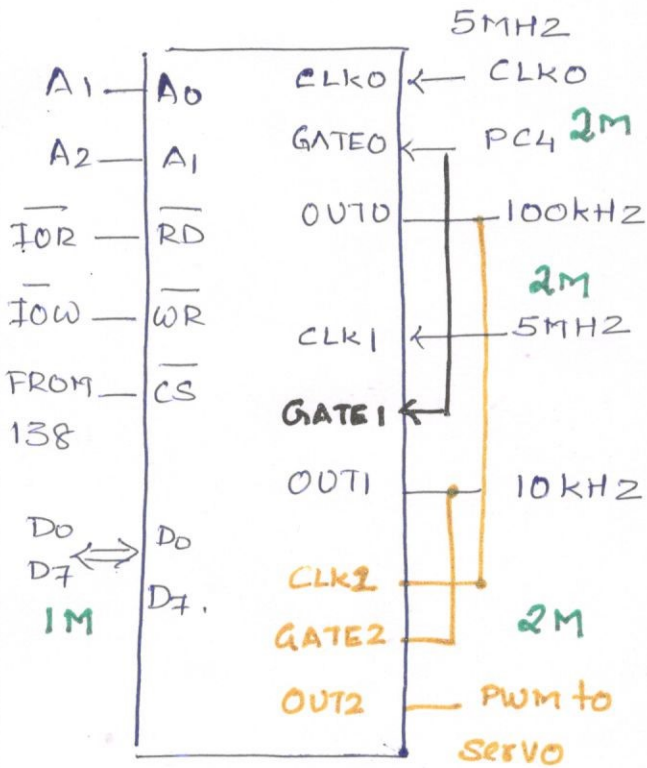

8254 Count of Timers for 10KHz PWM at 20%
60%

Timer 0 - 50

Timer 1 - 500

Timer 2 - 08

2M

8254 Initialization

```

mov al, 00110100
out 46h, al      1M
mov al, 01110100
out 46h, al      1M
mov al, 10110010
out 46h, al.     1M.
    
```

8254 Count of Timers for 10KHz PWM at 60%

Timer 0 - 50


Timer 1 - 500

Timer 2 - 04

2M

Q1e

8259 Interfacing

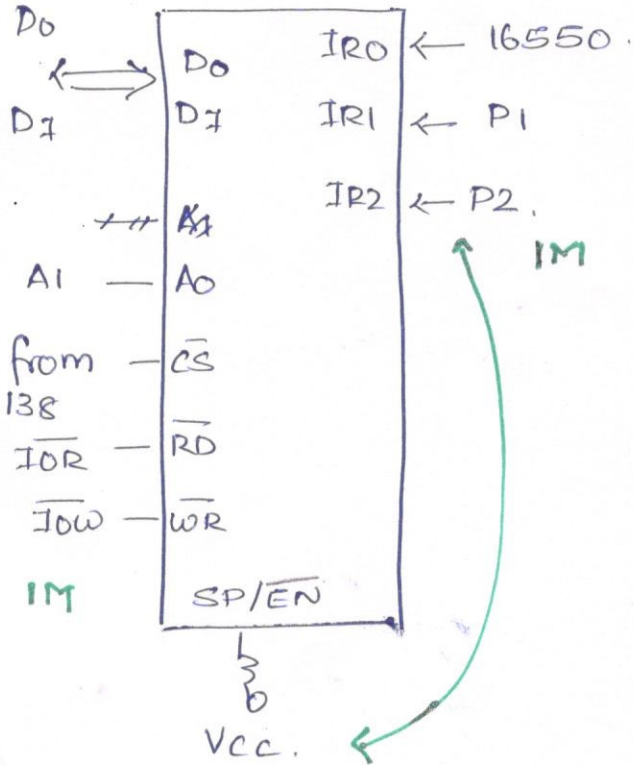

8259 Initialization

```
mov al, 00010011B
out 50h, al 2M

mov al, 60h
out 52h, al IM


mov al, 00000011B
out 52h, al 2M

mov al, 11111000B
out 52h, al IM
```


Q1f

16550 Interfacing

16550 Initialization

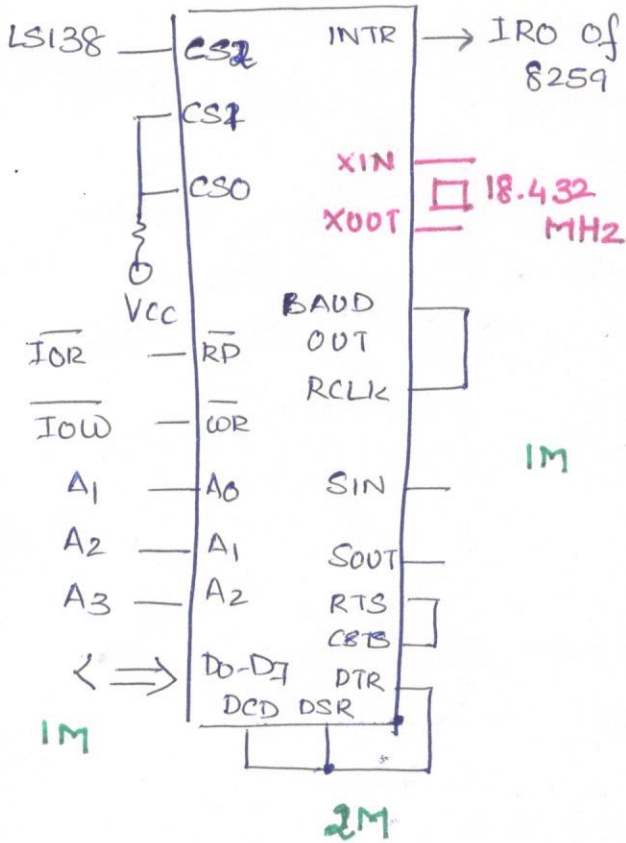

```
mov al, 10001011B
out 36h, al. IM
mov al, 60
out 30h, al
mov al, 00 2M
out 32h, al
mov al, 00001011B.
out 36h, al
mov al, 01000001B.
out 34h, al. IM
```