# PROTEUS SYSTEM DESIGN EXAMPLE



A 8086 based system checks a set of 8 switches (SW1- SW8) every 1 second and displays the no. of switch that is closed(assume only 1 switch is closed at a time) - if no switch is closed - 0 is displayed.

# SWITCH – SINGLE POLE DOUBLE THROW SWITCH



# INTERFACE TO SWITCH



 $\blacksquare PB_0 - PB_7 (SWI - SW8)$ 

## 7 SEGMENT DISPLAY

- I seven segment displays
- | |- 7447
- Requires 4-bit



#### I SEC INTERRUPT

Use 8253 as only that is available in proteus

Clock has to be generated using pulse generator using IOKHz – if a higher frequency is used – pulse will not be proper- as rise and fall time of pulse in proteus can be set to a minimum of I µs – and the rise and fall time are should be less than I % of frequency.



# INTERRUPT GENERATION





#### INTERFACE 8255, 8254 & 8259

- Fixed addressing
- Address
- 00 06<sub>H</sub> -8255
- 08<sub>H</sub> 0E<sub>H</sub> 8254
- 10<sub>H</sub> 12<sub>H</sub> 8259
- Incremental Addressing



#### INTERFACE MEMORY

- RAM minimum 2k chip- 4k
- ROM in proteus 7 is minimum 4k chip 8k
- ROMI 00000<sub>H</sub> 01FFF<sub>H</sub>
  - This is ok as proteus allows you to set reset address I have set it to 0000:0400(CS:IP)
  - This the area after IVT
- RAM 02000<sub>H</sub> 02FFF<sub>H</sub>











System Bus of 8086 (Address)





8086 Inputs

# Software







Use EMU 8086 for assembling – as it creates the read binary file to load to 8086 ROM